

# Alexandria University

Faculty of Engineering

Department of Electrical Communications and Electronics

---

## 8-bit Super Register

Digital Systems Design Lab Project

---

### Project Team Members

Student Name	Student ID
Elsayed Ashraf Bakry	23010293
Mohamed Ayman Elsaygh	23010730
Ahmed Bassem AboKila	24011105
Omar Ibrahim Elsagan	23010600
Mohamed Yasser Samak	24011107

**Course:** Digital Systems Design

Academic Year: 2025 – 2026

# Contents

1	Introduction	2
2	Complete VHDL Code	3
3	Store Operation (000)	4
4	Parallel Load Operation (001)	5
5	Shift Right Operation (010)	6
6	Shift Left Operation (011)	7
7	Rotate Right Operation (100)	8
8	Rotate Left Operation (101)	9
9	Count Up Operation (110)	10
10	Count Down Operation (111)	11
11	Control Signal Summary	12
12	Flag Operation	12
13	Conclusion	13

# **1 Introduction**

This report presents the design and implementation of an 8-bit Super Register using VHDL. The register is capable of performing eight different operations including storage, shifting, rotation, and counting. The operation is selected using a 3-bit control signal, and all operations are synchronized with the rising edge of the clock.

## 2 Complete VHDL Code

```
1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.numeric_std.all;
4
5 entity super_register is
6 port(
7     clk          : in  std_logic;
8     data_in       : in  std_logic_vector(7 downto 0);
9     data_sh_r     : in  std_logic;
10    data_sh_l     : in  std_logic;
11    control        : in  std_logic_vector(2 downto 0);
12    data_out       : out std_logic_vector(7 downto 0);
13    flag           : out std_logic
14 );
15 end super_register;
16
17 architecture behavior of super_register is
18 signal Q : std_logic_vector(7 downto 0);
19 begin
20 process(clk)
21 begin
22     if rising_edge(clk) then
23         case control is
24             when "000" => Q <= Q;
25             when "001" => Q <= data_in;
26             when "010" =>
27                 for i in 0 to 6 loop
28                     Q(i) <= Q(i+1);
29                 end loop;
30                 Q(7) <= data_sh_r;
31             when "011" =>
32                 for i in 0 to 6 loop
33                     Q(7-i) <= Q(6-i);
34                 end loop;
35                 Q(0) <= data_sh_l;
36             when "100" =>
37                 for i in 0 to 6 loop
38                     Q(i) <= Q(i+1);
39                 end loop;
40                 Q(7) <= Q(0);
41             when "101" =>
42                 for i in 0 to 6 loop
43                     Q(i+1) <= Q(i);
44                 end loop;
45                 Q(0) <= Q(7);
46             when "110" => Q <= std_logic_vector(unsigned(Q) + 1);
47             when "111" => Q <= std_logic_vector(unsigned(Q) - 1);
48             when others => Q <= Q;
49         end case;
50     end if;
51 end process;
52
53 data_out <= Q;
54 flag <= '1' when (Q = "00000000" or Q = "11111111") else '0';
55 end behavior;
```

### 3 Store Operation (000)

The register holds its current value without change.

```
1 when "000" => Q <= Q;
```

Listing 1: Hold Operation VHDL Code

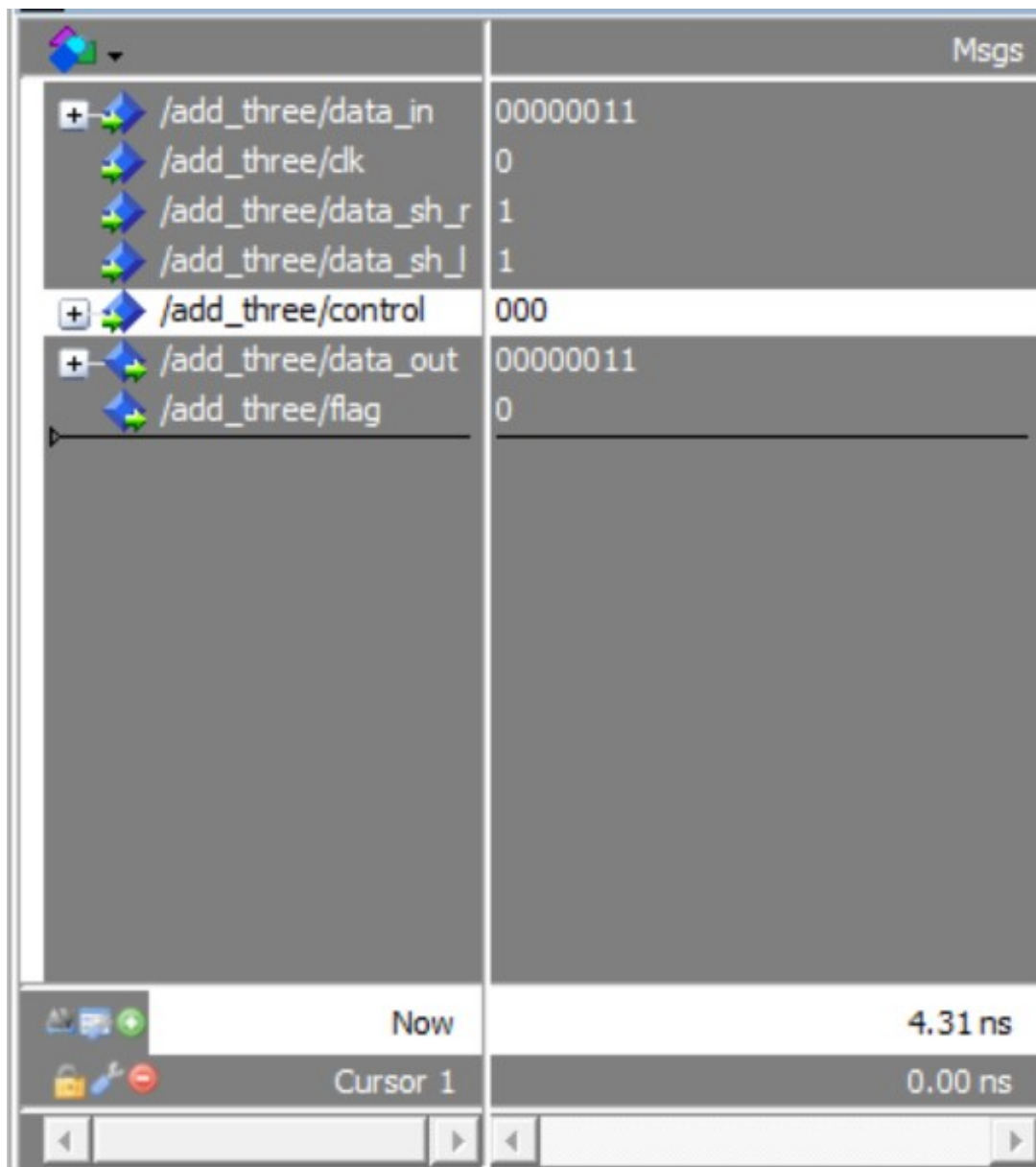


Figure 1: Simulation of Parallel Load Operation

**Note:** The hold operation maintains the current state of the register without any modification.

## 4 Parallel Load Operation (001)

Loads the input data into the register.

```
1 when "001" => Q <= data_in;
```

Listing 2: Parallel Load Operation VHDL Code

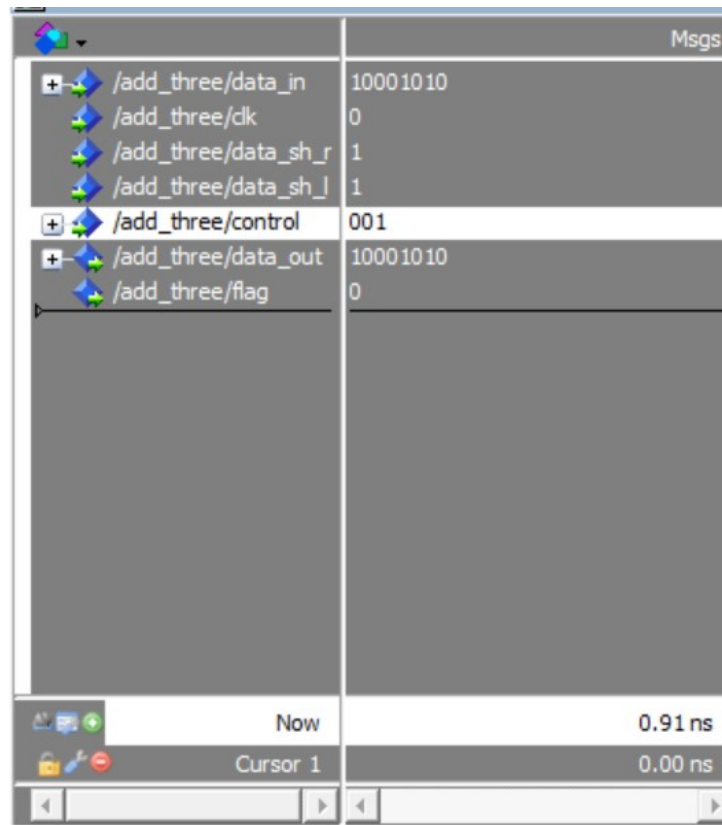


Figure 2: Simulation of Parallel Load Operation

**Explanation:** When control = "001", the register loads the 8-bit value from `data_in` on the rising edge of the clock.

## 5 Shift Right Operation (010)

Shifts all bits one position to the right. The most significant bit (MSB) receives the value from data\_sh\_r.

```
1 when "010" =>
2   for i in 0 to 6 loop
3     Q(i) <= Q(i+1);
4   end loop;
5   Q(7) <= data_sh_r;
```

Listing 3: Shift Right Operation VHDL Code

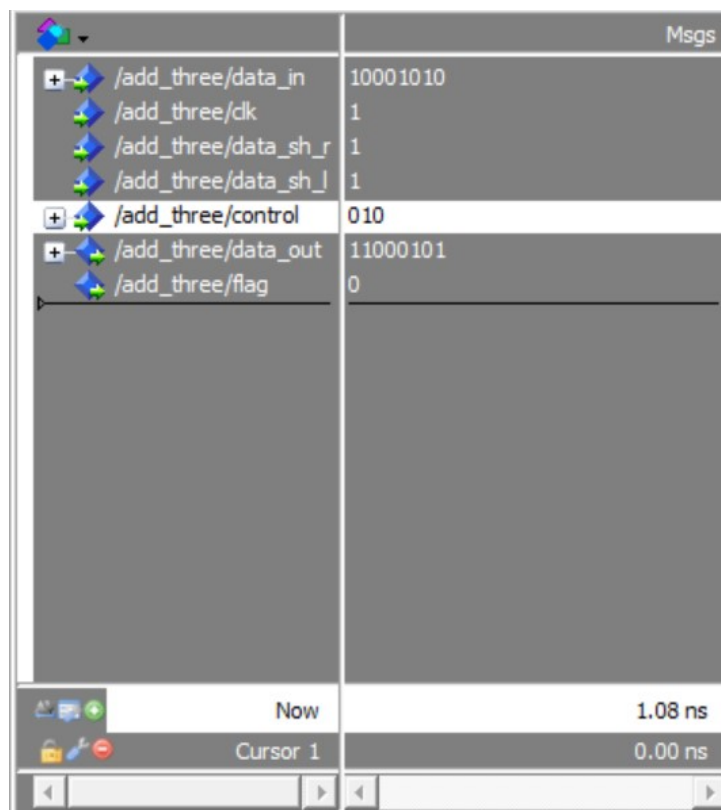


Figure 3: Simulation of Shift Right Operation

### Operation:

- Bit 0  $\leftarrow$  Bit 1
- Bit 1  $\leftarrow$  Bit 2
- ...
- Bit 6  $\leftarrow$  Bit 7
- Bit 7  $\leftarrow$  data\_sh\_r

## 6 Shift Left Operation (011)

Shifts all bits one position to the left. The least significant bit (LSB) receives the value from data\_sh\_1.

```
1 when "011" =>
2   for i in 0 to 6 loop
3     Q(7-i) <= Q(6-i);
4   end loop;
5   Q(0) <= data_sh_1;
```

Listing 4: Shift Left Operation VHDL Code

 


Figure 4: Simulation of Shift Left Operation

### Operation:

- Bit 7  $\leftarrow$  Bit 6
- Bit 6  $\leftarrow$  Bit 5
- ...
- Bit 1  $\leftarrow$  Bit 0
- Bit 0  $\leftarrow$  data\_sh\_1



## 7 Rotate Right Operation (100)

Performs circular right rotation. The least significant bit wraps around to become the most significant bit.

```
1 when "100" =>
2   for i in 0 to 6 loop
3     Q(i) <= Q(i+1);
4   end loop;
5   Q(7) <= Q(0);
```

Listing 5: Rotate Right Operation VHDL Code

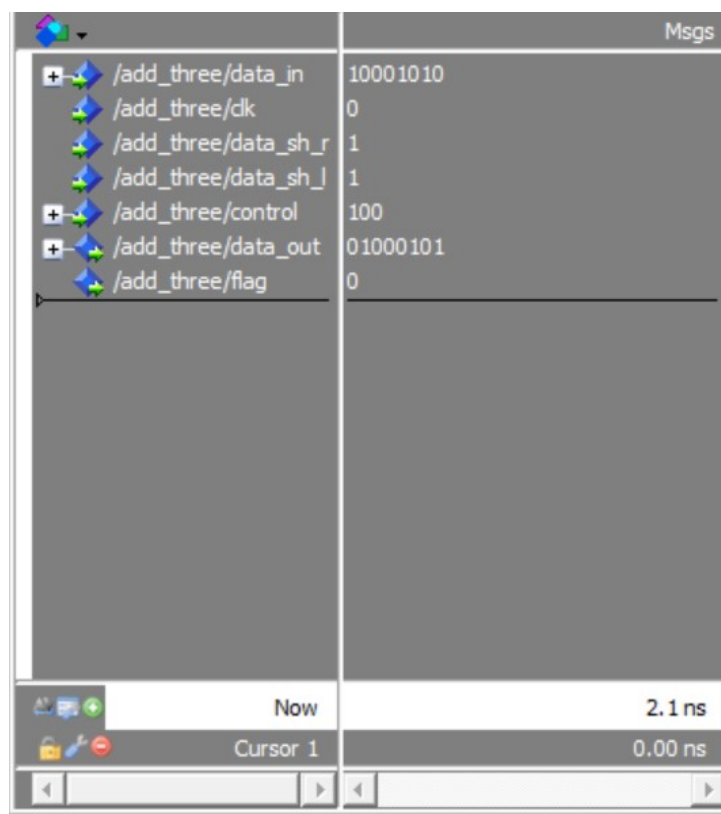


Figure 5: Simulation of Rotate Right Operation

### Operation:

- Bit 0  $\leftarrow$  Bit 1
- Bit 1  $\leftarrow$  Bit 2
- ...
- Bit 6  $\leftarrow$  Bit 7
- Bit 7  $\leftarrow$  Original Bit 0

## 8 Rotate Left Operation (101)

Performs circular left rotation. The most significant bit wraps around to become the least significant bit.

```
1 when "101" =>
2   for i in 0 to 6 loop
3     Q(i+1) <= Q(i);
4   end loop;
5   Q(0) <= Q(7);
```

Listing 6: Rotate Left Operation VHDL Code

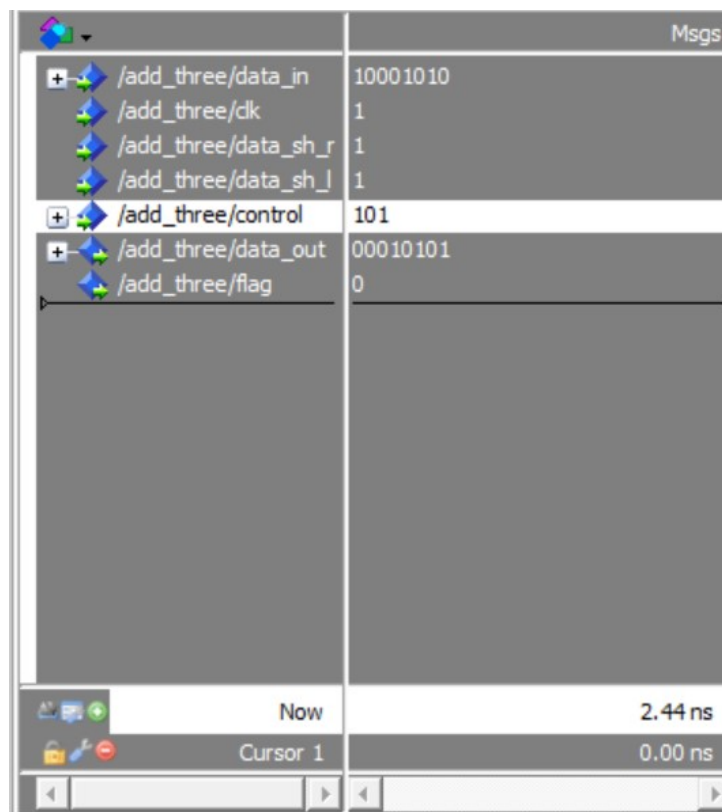


Figure 6: Simulation of Rotate Left Operation

### Operation:

- Bit 7  $\leftarrow$  Bit 6
- Bit 6  $\leftarrow$  Bit 5
- ...
- Bit 1  $\leftarrow$  Bit 0
- Bit 0  $\leftarrow$  Original Bit 7

## 9 Count Up Operation (110)

Increments the register value by one using unsigned arithmetic.

```
1 when "110" => Q <= std_logic_vector(unsigned(Q) + 1);
```

Listing 7: Count Up Operation VHDL Code

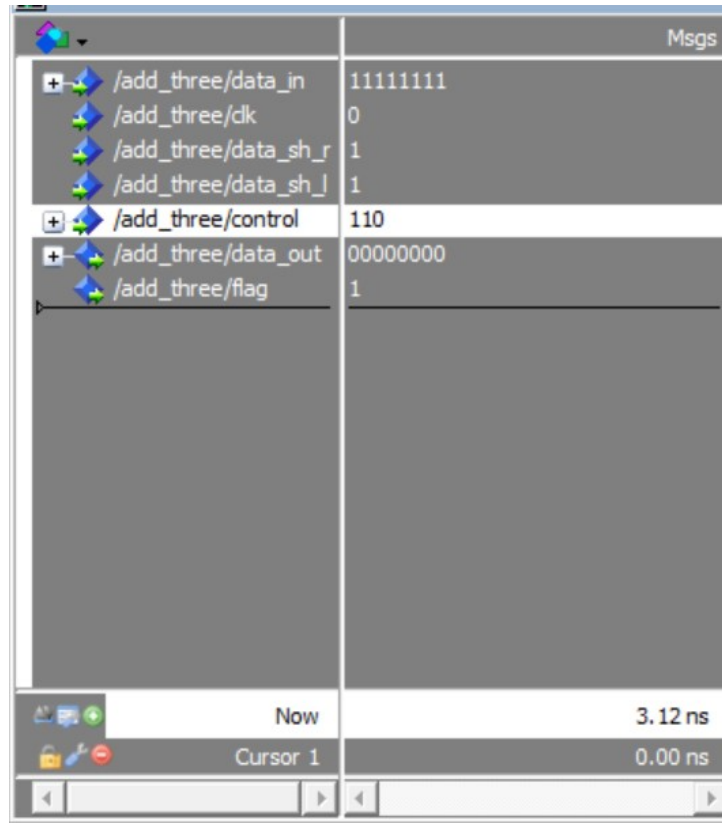


Figure 7: Simulation of Count Up Operation (with Flag Assertion)

**Note:** The flag signal becomes '1' when the register value reaches "11111111" and wraps to "00000000".

## 10 Count Down Operation (111)

Decrements the register value by one using unsigned arithmetic.

```
1 when "111" => Q <= std_logic_vector(unsigned(Q) - 1);
```

Listing 8: Count Down Operation VHDL Code

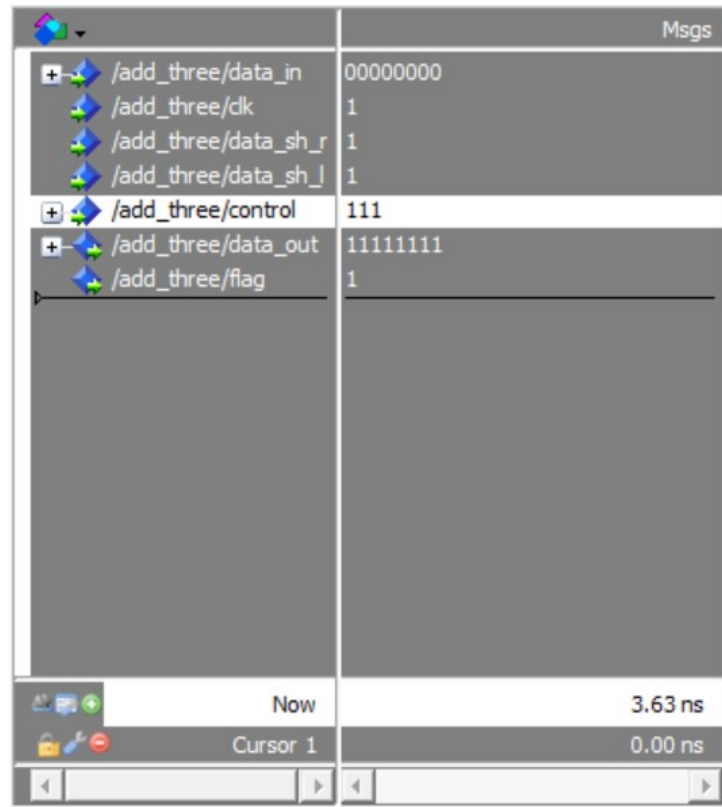


Figure 8: Simulation of Count Down Operation (with Flag Assertion)

**Note:** The flag signal becomes '1' when the register value reaches "00000000" and wraps to "11111111".

## 11 Control Signal Summary

Control	Operation	Description
000	Hold	Maintains current register value
001	Parallel Load	Loads <code>data_in</code> into register
010	Shift Right	Right shift with <code>data_sh_r</code> input
011	Shift Left	Left shift with <code>data_sh_l</code> input
100	Rotate Right	Circular right rotation
101	Rotate Left	Circular left rotation
110	Count Up	Increment register by one
111	Count Down	Decrement register by one

Table 1: Super Register Control Operations

## 12 Flag Operation

The flag signal indicates special conditions in the register. It is computed as follows:

```
1 flag <= '1' when (Q = "00000000" or Q = "11111111") else '0';
```

Listing 9: Flag Logic Implementation

### Flag Conditions:

- `flag = '1'` when register contains all zeros (00000000)
- `flag = '1'` when register contains all ones (11111111)
- `flag = '0'` for all other values

### Applications:

- Detecting overflow/underflow in counters
- Signaling end-of-sequence conditions
- Boundary detection in control algorithms

## 13 Conclusion

The 8-bit Super Register was successfully designed and implemented using VHDL. The design integrates multiple operations in a single synchronous circuit and was verified through simulation. The register can be easily extended or integrated into larger digital systems.

### **Key Features:**

- 8 different operations controlled by 3-bit control signal
- Synchronous operation on rising clock edge
- Flag output for boundary condition detection
- Support for serial data input during shifts
- Built-in up/down counter functionality

**Verification:** All operations were verified through simulation as shown in the included figures, confirming correct functionality for each control code.